

Digital Design and Computer Organisation Laboratory

3rd Semester, Academic Year 2025

Date:29-09-2025

Name: Aakash Desai	SRN:PES1UG24CS006	Section
		3A

Week Number: 6

Program Number: 1

TITLE: Write an iverilog program to design and implement a 2-bit up counter using JK flip flops.Generate the VVP output and simulation waveform using GTKWave.

Deliverables

- I. Verilog Code Screenshot
- II. Verilog VVP Output Screen Shot
- III. GTKWAVE Screenshot
- IV. Output Table to be completed and included

I.Verilog Code Snippet

- Main code

```

module jkff(input clk, input reset, input j, input k, output reg q);
    always @(posedge clk) begin
        if (reset)
            q <= 1'b0;           // synchronous reset
        else begin
            case ({j,k})
                2'b00: q <= q;           // no change
                2'b01: q <= 1'b0;       // reset
                2'b10: q <= 1'b1;       // set
                2'b11: q <= ~q;         // toggle
            endcase
        end
    end
endmodule

module up_counter_2bit(input clk, input reset, output [1:0] q);
    wire j0, k0, j1, k1;
    assign j0 = 1'b1;
    assign k0 = 1'b1;

    assign j1 = q[0];
    assign k1 = q[0];

    jkff jkff0 (.clk(clk), .reset(reset), .j(j0), .k(k0), .q(q[0]));
    jkff jkff1 (.clk(clk), .reset(reset), .j(j1), .k(k1), .q(q[1]));
endmodule

```

- Test Bench

```

module tb_up_counter_2bit;
    reg clk, reset;
    wire [1:0] q;

    up_counter_2bit uut(.clk(clk), .reset(reset), .q(q));

    initial clk = 0;
    always #5 clk = ~clk;

    initial begin
        $dumpfile("up_counter_jk.vcd");
        $dumpvars(0, tb_up_counter_2bit);
        $display("Time\tClk\tReset\tQ1Q0");
        $monitor("%0t\t%b\t%b\t%b%b", $time, clk, reset, q[1], q[0]);

        reset = 1; #10;    // apply reset
        reset = 0;         // release reset
        #60;

        reset = 1; #10;    // reset again
        reset = 0;         // release reset
        #40;

        $finish;
    end
endmodule


```

II Verilog VVP output ScreenShot

```
C:\iverilog\bin\Week6>vvp dsn
VCD info: dumpfile up_counter_jk.vcd opened for output.
```

Time	Clk	Reset	Q1Q0
0	0	1	xx
5	1	1	00
10	0	0	00
15	1	0	01
20	0	0	01
25	1	0	10
30	0	0	10
35	1	0	11
40	0	0	11
45	1	0	00
50	0	0	00
55	1	0	01
60	0	0	01
65	1	0	10
70	0	1	10
75	1	1	00
80	0	0	00
85	1	0	01
90	0	0	01
95	1	0	10
100	0	0	10
105	1	0	11
110	0	0	11
115	1	0	00
120	0	0	00

III GTKWave ScreenShot

 

IV Excitation Table

Current State		Next State		Flip Flops			
Q1	Q0	Q1	Q0	J1	K1	J0	K0
0	0	0	1	0	X	1	X
0	1	1	0	1	X	X	1
1	0	1	1	X	0	1	X
1	1	0	0	X	1	X	1

TITLE: Write an iverilog program to design and implement a 2-bit down counter using JK flip flops. Generate the VVP output and simulation waveform using GTKWave.

Deliverables

- I. Verilog Code Screenshot
- II. Verilog VVP Output Screen Shot
- III. GTKWAVE Screenshot
- IV. Output Table to be completed and included

I. Verilog Code Snippet

- Main Code

```
module jkff(input clk, input reset, input j, input k, output reg q);
    always @(posedge clk) begin
        if (reset)
            q <= 1'b0;          // synchronous reset
        else begin
            case ({j,k})
                2'b00: q <= q;      // no change
                2'b01: q <= 1'b0;    // reset
                2'b10: q <= 1'b1;    // set
                2'b11: q <= ~q;      // toggle
            endcase
        end
    end
endmodule

module down_counter_2bit(input clk, input reset, output [1:0] q);
    wire j0, k0, j1, k1;

    assign j0 = 1'b1;
    assign k0 = 1'b1;

    assign j1 = ~q[0];
    assign k1 = ~q[0];

    // instantiate two JK flip-flops
    jkff jkff0 (.clk(clk), .reset(reset), .j(j0), .k(k0), .q(q[0]));
    jkff jkff1 (.clk(clk), .reset(reset), .j(j1), .k(k1), .q(q[1]));
endmodule
```

- Test Bench

```
module tb_up_counter_2bit;
    reg clk, reset;
    wire [1:0] q;

    down_counter_2bit uut(.clk(clk), .reset(reset), .q(q));

    initial clk = 0;
    always #5 clk = ~clk;

    initial begin
        $dumpfile("up_counter_jk.vcd");
        $dumpvars(0, tb_up_counter_2bit);
        $display("Time\tClk\tReset\tQ1Q0");
        $monitor("%0t\t%b\t%b\t%b%b", $time, clk, reset, q[1], q[0]);

        reset = 1; #10;    // apply reset
        reset = 0;         // release reset
        #60;


        reset = 1; #10;    // reset again
        reset = 0;         // release reset
        #40;

        $finish;
    end
endmodule
```

II Verilog VVP ScreenShot

Time	Clk	Reset	Q1Q0
0	0	1	xx
5	1	1	00
10	0	0	00
15	1	0	11
20	0	0	11
25	1	0	10
30	0	0	10
35	1	0	01
40	0	0	01
45	1	0	00
50	0	0	00
55	1	0	11
60	0	0	11
65	1	0	10
70	0	1	10
75	1	1	00
80	0	0	00
85	1	0	11
90	0	0	11
95	1	0	10
100	0	0	10
105	1	0	01
110	0	0	01
115	1	0	00
120	0	0	00

III GTK wave Screenshot

 

IV Excitation Table

Current State		Next State		Flip Flops			
Q1	Q0	Q1	Q0	J1	K1	J0	K0
0	0	1	1	1	X	1	X
0	1	0	0	0	X	X	1
1	0	0	1	X	1	1	X
1	1	1	0	X	0	X	1

TITLE: Write an iverilog program to design and implement a 2-bit up-down counter using JK flip flops. Generate the VVP output and simulation waveform using GTKWave.

Deliverables

- I. Verilog Code Screenshot
 - II. Verilog VVP Output Screen Shot
 - III. GTKWAVE Screenshot
 - IV. Output Table to be completed and included
- I Iverilog code

```
module jkff(input clk, input reset, input j, input k, output reg q);
    always @(posedge clk) begin
        if (reset)
            q <= 1'b0;          // synchronous reset
        else begin
            case ({j,k})
                2'b00: q <= q;      // no change
                2'b01: q <= 1'b0;   // reset
                2'b10: q <= 1'b1;   // set
                2'b11: q <= ~q;     // toggle
            endcase
        end
    end
endmodule

module up_down_counter_2bit(input clk, input reset, input up_down, output [1:0] q);
    wire j0, k0, j1, k1;

    // LSB always toggles
    assign j0 = 1'b1;
    assign k0 = 1'b1;

    // MSB toggles condition depends on up_down
    // For UP -> toggle when q[0] = 1
    // For DOWN -> toggle when q[0] = 0
    assign j1 = (up_down) ? q[0] : ~q[0];
    assign k1 = (up_down) ? q[0] : ~q[0];

    // instantiate two JK flip-flops
    jkff jkff0 (.clk(clk), .reset(reset), .j(j0), .k(k0), .q(q[0]));
    jkff jkff1 (.clk(clk), .reset(reset), .j(j1), .k(k1), .q(q[1]));
endmodule
```

- Testbench

```
module tb_up_down_counter_2bit;
    reg clk, reset, up_down;
    wire [1:0] q;

    up_down_counter_2bit uut(.clk(clk), .reset(reset), .up_down(up_down), .q(q));

    initial clk = 0;
    always #5 clk = ~clk;

    initial begin
        $dumpfile("up_down_counter_jk.vcd");
        $dumpvars(0, tb_up_down_counter_2bit);
        $display("Time\tClk\tReset\tUD\tQ1Q0");
        $monitor("%0t\t%b\t%b\t%b\t%b%b", $time, clk, reset, up_down, q[1], q[0]);

        reset = 1; up_down = 1; #10;
        reset = 0;

        #40;


        up_down = 0;
        #40;

        $finish;
    end
endmodule
```

II VVP screenshot

```
C:\iverilog\bin\Week6>vvp dsn
VCD info: dumpfile up_down_counter_jk.vcd opened for output.
Time      Clk      Reset    UD      Q1Q0
0         0         1        1       xx
5         1         1        1       00
10        0         0        1       00
15        1         0        1       01
20        0         0        1       01
25        1         0        1       10
30        0         0        1       10
35        1         0        1       11
40        0         0        1       11
45        1         0        1       00
50        0         0        0       00
55        1         0        0       11
60        0         0        0       11
65        1         0        0       10
70        0         0        0       10
75        1         0        0       01
80        0         0        0       01
85        1         0        0       00
90        0         0        0       00
```

III GTKwave screenshot

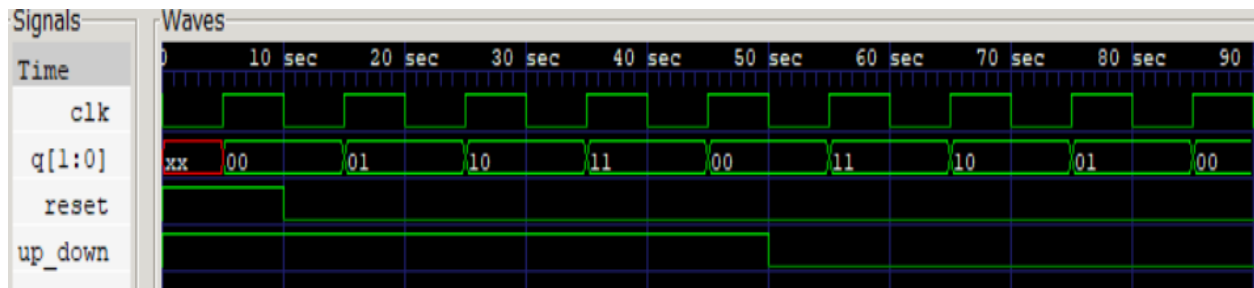

IV Characteristic Table

Mode Select	Current State		Next State		Flip Flops			
	Q1	Q0	Q1	Q0	J1	K1	J0	K0
0	0	0	0	1	0	X	1	X
1	0	0	1	1	1	X	1	X
0	0	1	1	0	1	X	X	1
1	0	1	0	0	0	X	X	1
0	1	0	1	1	X	0	1	X
1	1	0	0	1	X	1	1	X
0	1	1	0	0	X	1	X	1
1	1	1	1	0	X	0	X	1

TITLE: Write a verilog program to design a 2 bit ripple up counter using D flip flop. Generate the VVP output and simulation waveform using GTKWave.

Deliverables

- I. Verilog Code Screenshot
- II. Verilog VVP Output Screen Shot
- III. GTKWAVE Screenshot
- IV. Output Table to be completed and included

I.Verilog code

- Main code

```
module dff_async_reset(
    input clk,
    input reset,
    input d,
    output reg q
);
    always @(posedge clk or posedge reset) begin
        if (reset)
            q <= 1'b0; // Resets output to 0 immediately
        else
            q <= d;
        end
    endmodule

module ripple_up_counter_2bit(
    input clk,
    input reset,
    output [1:0] q
);
    wire nq0;
    assign nq0 = ~q[0];
    dff_async_reset dff0 (
        .clk(clk),
        .reset(reset),
        .d(~q[0]), // Connect D to ~Q to make it toggle
        .q(q[0])
    );

    dff_async_reset dff1 (
        .clk(nq0), // <-- The clock ripples from the previous stage
        .reset(reset), // <-- **CRITICAL FIX**: Reset is connected here too
        .d(~q[1]), // Connect D to ~Q to make it toggle
        .q(q[1])
    );
endmodule
```

- Test bench

```
module tb_ripple_up_counter_2bit;
    reg clk;
    reg reset;
    wire [1:0] q;
    ripple_up_counter_2bit uut (
        .clk(clk),
        .reset(reset),
        .q(q)
    );

    initial clk = 0;
    always #5 clk = ~clk;

    // Test sequence
    initial begin
        // Setup waveform dumping
        $dumpfile("ripple.vcd");
        $dumpvars(0, tb_ripple_up_counter_2bit);

        // Setup console monitoring
        $display("Time\tClk\tReset\tQ1Q0");
        $monitor("%0t\t%b\t%b\t%b%b", $time, clk, reset, q[1], q[0]);

        // 1. Assert reset at the beginning to initialize the counter
        reset = 1;
        #12; // Hold reset for a duration

        // 2. De-assert reset and let the counter run
        reset = 0;
        #80; // Run for 80 time units


        // 3. End the simulation
        $finish;
    end
endmodule
```

II VVP Screenshot

```
C:\iverilog\bin\Week6>vvp dsn
VCD info: dumpfile ripple.vcd opened for output.
```

Time	Clk	Reset	Q1Q0
0	0	1	00
5	1	1	00
10	0	1	00
12	0	0	00
15	1	0	01
20	0	0	01
25	1	0	10
30	0	0	10
35	1	0	11
40	0	0	11
45	1	0	00
50	0	0	00
55	1	0	01
60	0	0	01
65	1	0	10
70	0	0	10
75	1	0	11
80	0	0	11
85	1	0	00
90	0	0	00

III GTKWave output

 

IV State Transition Table

Current State		Next State	
Q1	Q0	Q1	Q0
0	0	0	1
0	1	1	0
1	0	1	1
1	1	0	0

TITLE: Write a verilog program to design and implement a 3 bit Ring Counter using D Flip flop. Generate the VVP output and simulation waveform using GTKWave.

Deliverables

- I. Verilog Code Screenshot
- II. Verilog VVP Output Screen Shot
- III. GTKWAVE Screenshot
- IV. Output Table to be completed and included

I Verilog Code

- Main code

```
module dff(input clk, input reset, input d, output reg q);
    always @(posedge clk) begin
        if (reset)
            q <= 1'b0;
        else
            q <= d;
        end
    endmodule

module ring_counter_3bit(input clk, input reset, output [2:0] q);
    wire [2:0] d;

    assign d[0] = q[2]; // last FF output fed to first FF
    assign d[1] = q[0];
    assign d[2] = q[1];

    dff dff0 (.clk(clk), .reset(reset), .d(d[0]), .q(q[0]));
    dff dff1 (.clk(clk), .reset(reset), .d(d[1]), .q(q[1]));
    dff dff2 (.clk(clk), .reset(reset), .d(d[2]), .q(q[2]));
endmodule
```


- Test bench

```

module tb_ring_counter_3bit;
    reg clk, reset;
    wire [2:0] q;

    ring_counter_3bit uut(.clk(clk), .reset(reset), .q(q));

    initial clk = 0;
    always #5 clk = ~clk; // 10 time unit period

    initial begin
        $dumpfile("ring_counter.vcd");
        $dumpvars(0, tb_ring_counter_3bit);

        $display("Time\tClk\tReset\tQ2Q1Q0");
        $monitor("%0t\t%b\t%b\t%b%b%b", $time, clk, reset, q[2], q[1], q[0]);

        reset = 1; #10;
        reset = 0;

        uut.dff0.q = 1'b1; // force Q0 = 1
        uut.dff1.q = 1'b0;
        uut.dff2.q = 1'b0;
        #80;
        $finish;
    end
endmodule

```

II VVP output Screenshot


```

C:\iverilog\bin\Week6>vvp dsn
VCD info: dumpfile ring_counter.vcd opened for output.

```

Time	Clk	Reset	Q2Q1Q0
0	0	1	xxx
5	1	1	000
10	0	0	001
15	1	0	010
20	0	0	010
25	1	0	100
30	0	0	100
35	1	0	001
40	0	0	001
45	1	0	010
50	0	0	010
55	1	0	100
60	0	0	100
65	1	0	001
70	0	0	001
75	1	0	010
80	0	0	010
85	1	0	100
90	0	0	100

III GTKwave output screenshot

 

IV Transition Table

Current State			D inputs			Next State		
Q2	Q1	Q0	D2	D1	D0	Q2	Q1	Q0
0	0	1	0	1	0	0	1	0
0	1	0	1	0	0	1	0	0
1	0	0	0	0	1	0	0	1
0	0	1	0	1	0	0	1	0

The counter has been initialized to a "one-hot" state of **001**.

TITLE: Write a verilog program to design and implement a 3 bit Johnson Counter using D Flip flop. Generate the VVP output and simulation waveform using GTKWave.

Deliverables

- I. Verilog Code Screenshot
- II. Verilog VVP Output Screen Shot
- III. GTKWAVE Screenshot
- IV. Output Table to be completed and included

I Verilog Code

Main code

```
module dff(input clk, input reset, input d, output reg q);
    always @(posedge clk) begin
        if (reset)
            q <= 1'b0;
        else
            q <= d;
        end
    endmodule

module johnson_counter_3bit(input clk, input reset, output [2:0] q);
    wire [2:0] d;

    assign d[0] = ~q[2];
    assign d[1] = q[0];
    assign d[2] = q[1];

    dff dff0 (.clk(clk), .reset(reset), .d(d[0]), .q(q[0]));
    dff dff1 (.clk(clk), .reset(reset), .d(d[1]), .q(q[1]));
    dff dff2 (.clk(clk), .reset(reset), .d(d[2]), .q(q[2]));
endmodule
```

Test Bench File

```
module tb_johnson_counter_3bit;
    reg clk, reset;
    wire [2:0] q;

    johnson_counter_3bit uut(.clk(clk), .reset(reset), .q(q));

    initial clk = 0;
    always #5 clk = ~clk; // 10 time unit period

    initial begin
        $dumpfile("johnson_counter.vcd");
        $dumpvars(0, tb_johnson_counter_3bit);


        $display("Time\tClk\tReset\tQ2Q1Q0");
        $monitor("%0t\t%b\t%b\t%b%b%", $time, clk, reset, q[2], q[1], q[0]);

        reset = 1; #10;
        reset = 0;
        #100;
        $finish;
    end
endmodule
```

II VVP Output Screenshot

```
C:\iverilog\bin\Week6>vvp dsn
VCD info: dumpfile johnson_counter.vcd opened for output.
Time      Clk      Reset    Q2Q1Q0
0         0         1        xxx
5         1         1        000
10        0         0        000
15        1         0        001
20        0         0        001
25        1         0        011
30        0         0        011
35        1         0        111
40        0         0        111
45        1         0        110
50        0         0        110
55        1         0        100
60        0         0        100
65        1         0        000
70        0         0        000
75        1         0        001
80        0         0        001
85        1         0        011
90        0         0        011
95        1         0        111
100       0         0        111
105       1         0        110
110       0         0        110
```

III GTKwave output screenshot

 

IV Table

The counter is initialized to an all-zero state.

Current State			D inputs			Next State		
Q2	Q1	Q0	D2	D1	D0	Q2	Q1	Q0
0	0	0	0	0	1	0	0	1
0	0	1	0	1	1	0	1	1
0	1	1	1	1	1	1	1	1
1	1	1	1	1	0	1	1	0
1	1	0	1	0	0	1	0	0
1	0	0	0	0	0	0	0	0
0	0	0	0	0	1	0	0	1

