

Digital Design and Computer Organisation Laboratory

3rd Semester, Academic Year 2025

Date:01-09-2025

Name: Aakash Desai	SRN:PES1UG24CS006	Section
		3A

Week Number: 4

Program Number: 1

TITLE: Write a verilog program to model 2:4 decoder with input enabled. Generate the VVP output and simulation waveform using GTKWave.

Deliverables

- I. Verilog Code Screenshot
- II. Verilog VVP Output Screen Shot
- III. GTKWAVE Screenshot
- IV. Output Table to be completed and included

I.Verilog Code Snippet

- Main code

```
module dec2to4 (  
    input wire [1:0] a,  
    input wire en,  
    output wire [3:0] y  
);  
  
    assign y[0] = en & ~a[1] & ~a[0];  
    assign y[1] = en & ~a[1] & a[0];  
    assign y[2] = en & a[1] & ~a[0];  
    assign y[3] = en & a[1] & a[0];  
  
endmodule
```


- Test Bench

```
module TB;  
    reg [1:0] A;  
    reg EN;  
    wire [3:0] Y;  
  
    dec2to4 newDEC (  
        .a(A),  
        .en(EN),  
        .y(Y)  
    );  
  
    initial begin  
        $dumpfile("DEC2_test.vcd");  
        $dumpvars(0, TB);  
        $monitor("Time=%0t | EN=%b | A=%b | Y=%b", $time, EN, A, Y);  
  
        EN = 1'b0; A = 2'b00; #5;  
        EN = 1'b1; A = 2'b00; #5;  
        EN = 1'b1; A = 2'b01; #5;  
        EN = 1'b1; A = 2'b10; #5;  
        EN = 1'b1; A = 2'b11; #5;  
        EN = 1'b0; A = 2'b10; #5;  
  
        $finish;  
    end  
endmodule
```

II Verilog VVP output ScreenShot

```
C:\iverilog\bin\Week4>vvp dsn
VCD info: dumpfile DEC2_test.vcd opened for output.
Time=0 | EN=0 | A=00 | Y=0000
Time=5 | EN=1 | A=00 | Y=0001
Time=10 | EN=1 | A=01 | Y=0010
Time=15 | EN=1 | A=10 | Y=0100
Time=20 | EN=1 | A=11 | Y=1000
Time=25 | EN=0 | A=10 | Y=0000
```

III GTKWave ScreenShot

 

IV Truth Table

E	A	B	D_0	D_1	D_2	D_3
1	X	X	1	1	1	1
0	0	0	0	1	1	1
0	0	1	1	0	1	1
0	1	0	1	1	0	1
0	1	1	1	1	1	0

TITLE: Write a verilog program to model 2:1 multiplexer.
Generate the VVP output and simulation waveform using GTKWave.

Deliverables

- I. Verilog Code Screenshot
- II. Verilog VVP Output Screen Shot
- III. GTKWAVE Screenshot
- IV. Output Table to be completed and included

I.Verilog Code Snippet

- Main Code

```
module mux2(  
    input wire i0,  
    input wire i1,  
    input wire j,  
    output wire o  
);  
    assign o = (j == 0) ? i0 : i1;  
endmodule
```

- TestBench

```
module TB;
    reg A, B, S;
    wire X;

    mux2 newMUX(
        .i0(A),
        .i1(B),
        .j(S),
        .o(X)
    );

    initial begin
        $dumpfile("MUX2_test.vcd");
        $dumpvars(0, TB);
        $monitor("Time=%0t | S=%b | A=%b | B=%b | X=%b", $time, S, A, B, X);


        // Test all combinations
        A = 1'b0; B = 1'b0; S = 1'b0; #5;
        A = 1'b0; B = 1'b0; S = 1'b1; #5;
        A = 1'b0; B = 1'b1; S = 1'b0; #5;
        A = 1'b0; B = 1'b1; S = 1'b1; #5;
        A = 1'b1; B = 1'b0; S = 1'b0; #5;
        A = 1'b1; B = 1'b0; S = 1'b1; #5;
        A = 1'b1; B = 1'b1; S = 1'b0; #5;
        A = 1'b1; B = 1'b1; S = 1'b1; #5;

        $finish;
    end
endmodule
```

II Verilog VVP ScreenShot

```
C:\iverilog\bin\Week4>vvp dsn
VCD info: dumpfile MUX2_test.vcd opened for output.
Time=0 | S=0 | A=0 | B=0 | X=0
Time=5 | S=1 | A=0 | B=0 | X=0
Time=10 | S=0 | A=0 | B=1 | X=0
Time=15 | S=1 | A=0 | B=1 | X=1
Time=20 | S=0 | A=1 | B=0 | X=1
Time=25 | S=1 | A=1 | B=0 | X=0
Time=30 | S=0 | A=1 | B=1 | X=1
Time=35 | S=1 | A=1 | B=1 | X=1
```

III GTK wave Screenshot

 

IV Truth Table

i_0	i_1	j	y
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

TITLE: Write a verilog program to model 4:1 multiplexer.
Generate the VVP output and simulation waveform using GTKWave.

Deliverables

- I. Verilog Code Screenshot
 - II. Verilog VVP Output Screen Shot
 - III. GTKWAVE Screenshot
 - IV. Output Table to be completed and included
- I lverilog code

```
module mux4(  
    input wire i0,  
    input wire i1,  
    input wire i2,  
    input wire i3,  
    input wire [1:0] sel,  
    output wire o  
);  
    assign o = (sel == 2'b00) ? i0 :  
                (sel == 2'b01) ? i1 :  
                (sel == 2'b10) ? i2 :  
                i3;  
endmodule
```


- Testbench

```
module TB;
    reg A, B, C, D;
    reg [1:0] S;
    wire X;

    mux4 newMUX(
        .i0(A),
        .i1(B),
        .i2(C),
        .i3(D),
        .sel(S),
        .o(X)
    );

    initial begin
        $dumpfile("MUX4_test.vcd");
        $dumpvars(0, TB);
        $monitor("Time=%0t | S=%b | A=%b | B=%b | C=%b | D=%b | X=%b", $time, S, A, B, C, D, X);


        A=0; B=0; C=0; D=0; S=2'b00; #5;
        A=0; B=1; C=0; D=0; S=2'b01; #5;
        A=1; B=0; C=0; D=0; S=2'b10; #5;
        A=1; B=1; C=1; D=0; S=2'b11; #5;
        A=0; B=1; C=1; D=1; S=2'b10; #5;
        A=1; B=0; C=1; D=1; S=2'b01; #5;

        $finish;
    end
endmodule
```

II VVP screenshot

```
C:\iverilog\bin\Week4>vvp dsn
VCD info: dumpfile MUX4_test.vcd opened for output.
Time=0 | S=00 | A=0 | B=0 | C=0 | D=0 | X=0
Time=5 | S=01 | A=0 | B=1 | C=0 | D=0 | X=1
Time=10 | S=10 | A=1 | B=0 | C=0 | D=0 | X=0
Time=15 | S=11 | A=1 | B=1 | C=1 | D=0 | X=0
Time=20 | S=10 | A=0 | B=1 | C=1 | D=1 | X=1
Time=25 | S=01 | A=1 | B=0 | C=1 | D=1 | X=0
```

III GTKwave screenshot

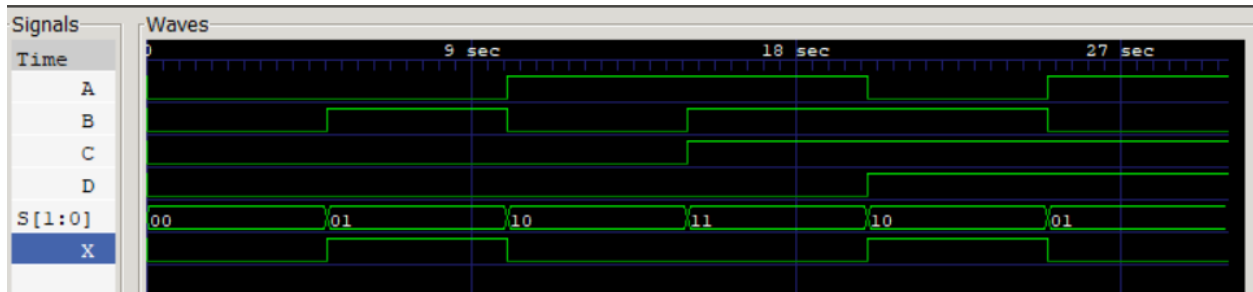

IV Truth Table

S_1	S_0	Y
0	0	I_0
0	1	I_1
1	0	I_2
1	1	I_3

(b) Function table

TITLE: Write a verilog program to model 1:4 demultiplexer.
Generate the VVP output and simulation waveform using GTKWave.

Deliverables

- I. Verilog Code Screenshot
- II. Verilog VVP Output Screen Shot
- III. GTKWAVE Screenshot
- IV. Output Table to be completed and included

I.Verilog code

- Main code

```
module demux1to4(  
    input wire i,  
    input wire [1:0] sel,  
    output wire y0, y1, y2, y3  
);  
    assign y0 = (sel == 2'b00) ? i : 1'b0;  
    assign y1 = (sel == 2'b01) ? i : 1'b0;  
    assign y2 = (sel == 2'b10) ? i : 1'b0;  
    assign y3 = (sel == 2'b11) ? i : 1'b0;  
endmodule  
|
```

- Test bench

```
module TB;
    reg IN;
    reg [1:0] S;
    wire Y0, Y1, Y2, Y3;

    demux1to4 newDEMUX(
        .i(IN),
        .sel(S),
        .y0(Y0),
        .y1(Y1),
        .y2(Y2),
        .y3(Y3)
    );

    initial begin
        $dumpfile("DEMUX1to4_test.vcd");
        $dumpvars(0, TB);
        $monitor("Time=%0t | S=%b | IN=%b | Y0=%b | Y1=%b | Y2=%b | Y3=%b", $time, S, IN, Y0, Y1, Y2, Y3);


        IN = 1'b0; S = 2'b00; #5;
        IN = 1'b1; S = 2'b00; #5;
        IN = 1'b1; S = 2'b01; #5;
        IN = 1'b1; S = 2'b10; #5;
        IN = 1'b1; S = 2'b11; #5;
        IN = 1'b0; S = 2'b10; #5;

        $finish;
    end
endmodule
```

II VVP Screenshot

```
C:\iverilog\bin\Week4>vvp dsn
VCD info: dumpfile DEMUX1to4_test.vcd opened for output.
Time=0 | S=00 | IN=0 | Y0=0 | Y1=0 | Y2=0 | Y3=0
Time=5 | S=00 | IN=1 | Y0=1 | Y1=0 | Y2=0 | Y3=0
Time=10 | S=01 | IN=1 | Y0=0 | Y1=1 | Y2=0 | Y3=0
Time=15 | S=10 | IN=1 | Y0=0 | Y1=0 | Y2=1 | Y3=0
Time=20 | S=11 | IN=1 | Y0=0 | Y1=0 | Y2=0 | Y3=1
Time=25 | S=10 | IN=0 | Y0=0 | Y1=0 | Y2=0 | Y3=0
```

III GTKWave output

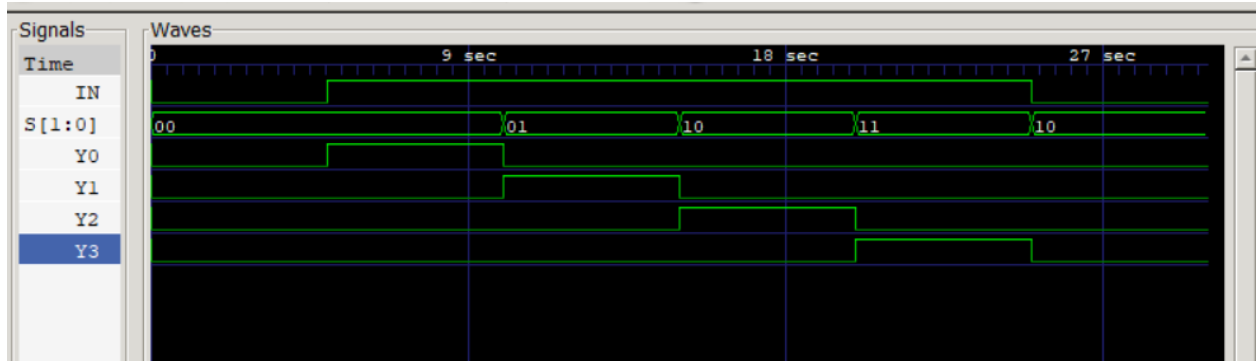

IV Truth Table

E	A	B	D0	D1	D2	D3
1	X	X	1	1	1	1
0	0	0	0	1	1	1
0	0	1	1	0	1	1
0	1	0	1	1	0	1
0	1	1	1	1	1	0

TITLE: Write a verilog program to model 1:2 demultiplexer.
Generate the VVP output and simulation waveform using GTKWave.

Deliverables

- I. Verilog Code Screenshot
- II. Verilog VVP Output Screen Shot
- III. GTKWAVE Screenshot
- IV. Output Table to be completed and included

I Verilog Code

- Main code

```
module demux1to2(  
    input wire i,  
    input wire sel,  
    output wire y0, y1  
);  
    assign y0 = (sel == 0) ? i : 1'b0;  
    assign y1 = (sel == 1) ? i : 1'b0;  
endmodule
```

- Test bench

```
module TB;
    reg IN;
    reg S;
    wire Y0, Y1;

    demux1to2 newDEMUX(
        .i(IN),
        .sel(S),
        .y0(Y0),
        .y1(Y1)
    );

    initial begin
        $dumpfile("DEMUX1to2_test.vcd");
        $dumpvars(0, TB);
        $monitor("Time=%0t | S=%b | IN=%b | Y0=%b | Y1=%b", $time, S, IN, Y0, Y1);


        IN = 1'b0; S = 1'b0; #5;
        IN = 1'b1; S = 1'b0; #5;
        IN = 1'b1; S = 1'b1; #5;
        IN = 1'b0; S = 1'b1; #5;

        $finish;
    end
endmodule
```

II VVP output Screenshot

```
C:\iverilog\bin\Week4>vvp dsn
VCD info: dumpfile DEMUX1to2_test.vcd opened for output.
Time=0 | S=0 | IN=0 | Y0=0 | Y1=0
Time=5 | S=0 | IN=1 | Y0=1 | Y1=0
Time=10 | S=1 | IN=1 | Y0=0 | Y1=1
Time=15 | S=1 | IN=0 | Y0=0 | Y1=0
```

III GTKwave output screenshot

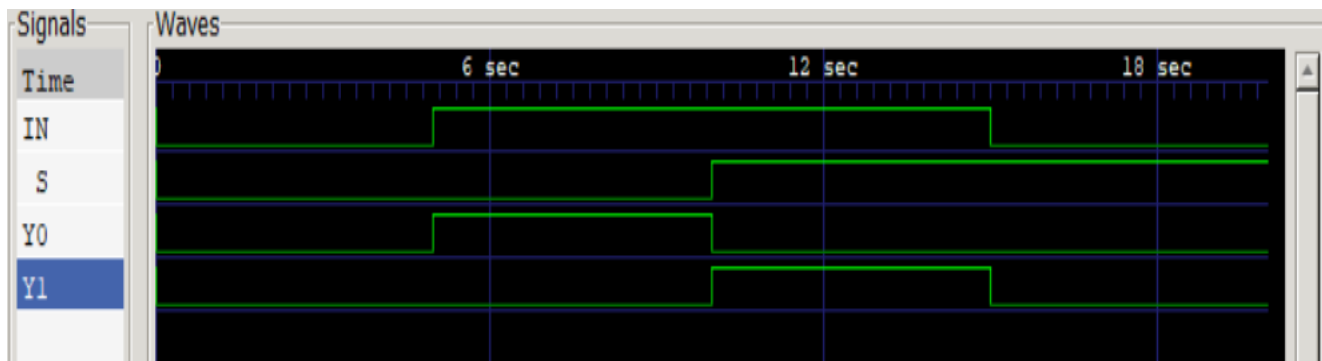

IV Truth Table

i (IN)	sel (S)	y0	y1
0	x	0	0
1	0	1	0
1	1	0	1

TITLE: Write a verilog program to model 4:2 encoder with input enabled. Generate the VVP output and simulation waveform using GTKWave.

Deliverables

- I. Verilog Code Screenshot
- II. Verilog VVP Output Screen Shot
- III. GTKWAVE Screenshot
- IV. Output Table to be completed and included

I Verilog Code Screenshot

- Main code

```
module enc4to2(  
    input wire [3:0] d,  
    input wire en,  
    output wire [1:0] y,  
    output wire valid  
);  
|  
    assign y[1] = en & (d[3] | d[2]);  
    assign y[0] = en & (d[3] | d[1]);  
    assign valid = en & (d[3] | d[2] | d[1] | d[0]);  
  
endmodule
```

- Test Bench

```
module TB;
    reg [3:0] D;
    reg EN;
    wire [1:0] Y;
    wire VALID;

    enc4to2 newENC(
        .d(D),
        .en(EN),
        .y(Y),
        .valid(VALID)
    );

    initial begin
        $dumpfile("ENC4to2_test.vcd");
        $dumpvars(0, TB);
        $monitor("Time=%0t | EN=%b | D=%b | Y=%b | VALID=%b", $time, EN, D, Y, VALID);


        EN = 1'b0; D = 4'b0000; #5;
        EN = 1'b1; D = 4'b0000; #5;
        EN = 1'b1; D = 4'b0001; #5;
        EN = 1'b1; D = 4'b0010; #5;
        EN = 1'b1; D = 4'b0100; #5;
        EN = 1'b1; D = 4'b1000; #5;
        EN = 1'b0; D = 4'b1010; #5;

        $finish;
    end
endmodule
```

II VVP screenshot

```
C:\iverilog\bin\Week4>vvp dsn
VCD info: dumpfile ENC4to2_test.vcd opened for output.
Time=0 | EN=0 | D=0000 | Y=00 | VALID=0
Time=5 | EN=1 | D=0000 | Y=00 | VALID=0
Time=10 | EN=1 | D=0001 | Y=00 | VALID=1
Time=15 | EN=1 | D=0010 | Y=01 | VALID=1
Time=20 | EN=1 | D=0100 | Y=10 | VALID=1
Time=25 | EN=1 | D=1000 | Y=11 | VALID=1
Time=30 | EN=0 | D=1010 | Y=00 | VALID=0
```

III GTKwave output

 

IV Truth Table

Inputs				Output	
D ₃	D ₂	D ₁	D ₀	B	A
0	0	0	0	X	X
0	0	0	1	0	0
0	0	1	X	0	1
0	1	X	X	1	0
1	X	X	X	1	1