

Digital Design and Computer Organisation Laboratory

3rd Semester, Academic Year 2025

Date:08-09-2025

Name: Aakash Desai	SRN:PES1UG24CS006	Section
		3A

Week Number: 5

Program Number: 1

TITLE: Write a verilog program to model a D Flip-flop.
Generate the VVP output and simulation waveform using
GTKWave.

Deliverables

- I. Verilog Code Screenshot
- II. Verilog VVP Output Screen Shot
- III. GTKWAVE Screenshot
- IV. Output Table to be completed and included

I.Verilog Code Snippet

- Main code

```
module dff (  
    input wire D,  
    input wire clk,  
    input wire rst,  
    output reg Q  
);  
always @(posedge clk or posedge rst) begin  
    if (rst)  
        Q <= 1'b0; // Asynchronous reset  
    else  
        Q <= D;    // Capture D on rising edge of clock  
    end  
endmodule
```

- Test Bench


```
module tb_dff;  
    reg D;  
    reg CLK;  
    reg RST;  
    wire Q;  
  
    dff newD(.D(D), .clk(CLK), .rst(RST), .Q(Q));  
    initial begin  
        CLK = 1'b0;  
        forever #5 CLK = ~CLK; // 10 time units period  
    end  
    initial begin  
        $dumpfile("dff.vcd");  
        $dumpvars(0, tb_dff);  
    end  
    initial begin  
        RST = 1'b1; D = 1'b0; #9;  
        RST = 1'b0;          #6;  
        D = 1'b1; #7;  
        D = 1'b0; #9;  
        D = 1'b1; #11;  
        D = 1'b0; #6;  
        RST = 1'b1; #5; RST = 1'b0; #15;  
        D = 1'b1; #12;  
        D = 1'b0; #8;  
        $finish;  
    end  
    initial begin  
        #200 $finish;  
    end  
    initial begin  
        $display("Time\tRST\tCLK\tD\tQ");  
        $monitor("%0t\t%b\t%b\t%b\t%b", $time, RST, CLK, D, Q);  
    end  
endmodule
```

II Verilog VVP output ScreenShot

VCD info: dumpfile dff.vcd opened for output.

Time	RST	CLK	D	Q
0	1	0	0	0
5	1	1	0	0
9	0	1	0	0
10	0	0	0	0
15	0	1	1	1
20	0	0	1	1
22	0	0	0	1
25	0	1	0	0
30	0	0	0	0
31	0	0	1	0
35	0	1	1	1
40	0	0	1	1
42	0	0	0	1
45	0	1	0	0
48	1	1	0	0
50	1	0	0	0
53	0	0	0	0
55	0	1	0	0
60	0	0	0	0
65	0	1	0	0
68	0	1	1	0
70	0	0	1	0
75	0	1	1	1
80	0	0	0	1
85	0	1	0	0

III GTKWave ScreenShot

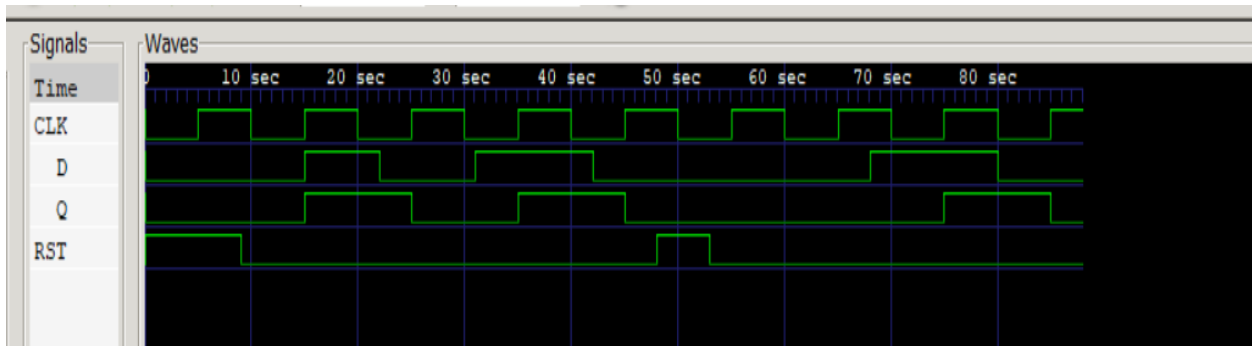

IV Characteristic Table

characteristic Table

Q_n	D	Q_{n+1}
0	0	0
0	1	1
1	0	0
1	1	1

$Q_{n+1} = D$

TITLE: Write a verilog program to model T Flip-flop.

Generate the VVP output and simulation waveform using GTKWave.

Deliverables

- I. Verilog Code Screenshot
- II. Verilog VVP Output Screen Shot
- III. GTKWAVE Screenshot
- IV. Output Table to be completed and included

I.Verilog Code Snippet

- Main Code

```
module t_ff (input wire T, input wire clk, input wire rst, output reg Q);
always @(posedge clk) begin
    Q = 1'b0;
    if (rst)
        Q <= 1'b0;
    else if (T)
        Q <= ~Q;
    else
        Q <= Q;
end
endmodule
```

- Test Bench

```

module TB_T;
reg T;
reg CLK;
reg RST;
wire Q;

t_ff newT (.T(T), .clk(CLK), .rst(RST), .Q(Q));

initial begin
    CLK = 1'b0;
    forever #5 CLK = ~ CLK;
end

initial begin
    $dumpfile("t_ff.vcd");
    $dumpvars(0,TB_T);
end

initial begin
    $monitor ("Time=%0t | RST=%b | T=%b | Q=%b", $time, RST, T, Q);
end

initial begin
    RST = 1'b1; T=1'b0; #7;
    RST = 1'b0;          #8;

    T= 1'b0; #20;    //hold
    T = 1'b1; #40;    //toggle
    T = 1'b0; #20;    //hold
    RST = 1'b1; #6;
    RST = 1'b0; #14;


    $finish;
end
endmodule

```

II Verilog VVP ScreenShot

Time=0	RST=1	T=0	Q=x
Time=5	RST=1	T=0	Q=0
Time=7	RST=0	T=0	Q=0
Time=35	RST=0	T=1	Q=1
Time=45	RST=0	T=1	Q=1
Time=55	RST=0	T=1	Q=1
Time=65	RST=0	T=1	Q=1
Time=75	RST=0	T=0	Q=0
Time=95	RST=1	T=0	Q=0
Time=101	RST=0	T=0	Q=0

III GTK wave Screenshot

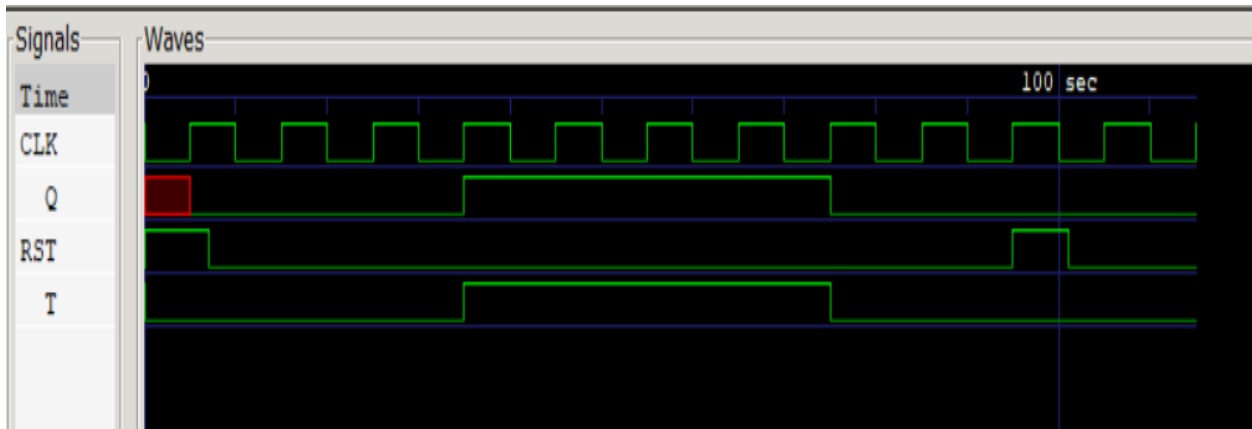

IV Truth Table

Truth Table

CLK	T	Q_{n+1}
↑	0	Q_n
↑	1	$\overline{Q_n}$

TITLE: Write a verilog program to model J-K Flip Flop. Generate the VVP output and simulation waveform using GTKWave.

Deliverables

- I. Verilog Code Screenshot
 - II. Verilog VVP Output Screen Shot
 - III. GTKWAVE Screenshot
 - IV. Output Table to be completed and included
- I Verilog code

```
module jk_ff(  
    input wire j,  
    input wire k,  
    input wire clk,  
    input wire rst,  
    output reg q  
);  
    always @(posedge clk or posedge rst) begin  
        if (rst)  
            q <= 1'b0;  
        else begin  
            case ({j,k})  
                2'b00: q <= q; |  
                2'b01: q <= 1'b0;  
                2'b10: q <= 1'b1;  
                2'b11: q <= ~q;  
            endcase  
        end  
    end  
endmodule
```


- Testbench


```
module tb_jk;
    reg J, K, CLK, RST;
    wire Q;
    jk_ff uut (
        .j(J),
        .k(K),
        .clk(CLK),
        .rst(RST),
        .q(Q)
    );
    initial begin
        CLK = 0;
        forever #5 CLK = ~CLK;
    end
    initial begin
        $dumpfile("jk.vcd");
        $dumpvars(0, tb_jk);
    end
    initial begin
        RST = 1; J = 0; K = 0; #12;
        RST = 0;
        J = 0; K = 0; #10;
        J = 0; K = 1; #10;
        J = 1; K = 0; #10;
        J = 1; K = 1; #10;
        J = 1; K = 1; #10;
        J = 0; K = 1; #10;
        J = 1; K = 0; #10;
        $finish;
    end
    initial begin
        $display("Time\tRST\tCLK\tJ\tK\tQ");
        $monitor("%0t\t%b\t%b\t%b\t%b\t%b", $time, RST, CLK, J, K, Q);
    end
endmodule
```

II VVP screenshot

```
C:\iverilog\bin\Week5>vvp dsn
VCD info: dumpfile jk.vcd opened for output.
```

Time	RST	CLK	J	K	Q
0	1	0	0	0	0
5	1	1	0	0	0
10	1	0	0	0	0
12	0	0	0	0	0
15	0	1	0	0	0
20	0	0	0	0	0
22	0	0	0	1	0
25	0	1	0	1	0
30	0	0	0	1	0
32	0	0	1	0	0
35	0	1	1	0	1
40	0	0	1	0	1
42	0	0	1	1	1
45	0	1	1	1	0
50	0	0	1	1	0
55	0	1	1	1	1
60	0	0	1	1	1
62	0	0	0	1	1
65	0	1	0	1	0
70	0	0	0	1	0
72	0	0	1	0	0
75	0	1	1	0	1
80	0	0	1	0	1

III GTKwave screenshot

 

IV Characteristic Table

characteristics table

Q_n	J	K	Q_{n+1}
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

$Q_{n+1} = J\bar{Q}_n + \bar{K}Q_n$

TITLE: Write a verilog program to model SR Flip Flop.
Generate the VVP output and simulation waveform using GTKWave.

Deliverables

- I. Verilog Code Screenshot
- II. Verilog VVP Output Screen Shot
- III. GTKWAVE Screenshot
- IV. Output Table to be completed and included

I.Verilog code

- Main code

```
module sr_ff(  
    input wire s,  
    input wire r,  
    input wire clk,  
    input wire rst,  
    output reg q  
);  
always @(posedge clk or posedge rst) begin  
    if (rst)  
        q <= 1'b0;  
    else begin  
        case ({s,r})  
            2'b00: q <= q;  
            2'b01: q <= 1'b0;  
            2'b10: q <= 1'b1;  
            2'b11: q <= 1'bx;  
        endcase  
    end  
end  
endmodule
```


- Test bench

```
module tb_sr_ff;
    reg s, r;
    reg clk, rst;
    wire q;
    sr_ff uut(
        .s(s),
        .r(r),
        .clk(clk),
        .rst(rst),
        .q(q)
    );
    initial clk = 0;
    always #5 clk = ~clk;
    initial begin
        $dumpfile("sr_ff.vcd");
        $dumpvars(0, tb_sr_ff);
        s = 0; r = 0; rst = 1;
        #10 rst = 0;
        s = 0; r = 0; #10;
        s = 1; r = 0; #10;
        s = 0; r = 1; #10;
        s = 1; r = 1; #10;
        s = 0; r = 0; #10;
        s = 1; r = 0; #10;
        s = 0; r = 1; #10;
        s = 0; r = 0; #10;
        $finish;
    end
    initial begin
        $monitor("Time=%0t | S=%b R=%b | Q=%b", $time, s, r, q);
    end
endmodule
```

II VVP Screenshot

```
C:\iverilog\bin\Week5>vvp dsn
VCD info: dumpfile sr_ff.vcd opened for output.
Time=0 | S=0 R=0 | Q=0
Time=20 | S=1 R=0 | Q=0
Time=25 | S=1 R=0 | Q=1
Time=30 | S=0 R=1 | Q=1
Time=35 | S=0 R=1 | Q=0
Time=40 | S=1 R=1 | Q=0
Time=45 | S=1 R=1 | Q=x
Time=50 | S=0 R=0 | Q=x
Time=60 | S=1 R=0 | Q=x
Time=65 | S=1 R=0 | Q=1
Time=70 | S=0 R=1 | Q=1
Time=75 | S=0 R=1 | Q=0
Time=80 | S=0 R=0 | Q=0
```

III GTKWave output

 

IV Truth Table

characteristics table

S	R	Q_n	Q_{n+1}
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	X
1	1	1	X

TITLE: Write a verilog program to design and implement a D flip flop using a T flip flop. Generate the VVP output and simulation waveform using GTKWave.

Deliverables

- I. Verilog Code Screenshot
- II. Verilog VVP Output Screen Shot
- III. GTKWAVE Screenshot
- IV. Output Table to be completed and included

I Verilog Code

- Main code

```
module t_ff(
    input wire t,
    input wire clk,
    input wire rst,
    output reg q
);
    always @(posedge clk or posedge rst) begin
        if (rst)
            q <= 1'b0;
        else if (t)
            q <= ~q;
        else
            q <= q;
        end
    endmodule
module d_ff_using_t(
    input wire d,
    input wire clk,
    input wire rst,
    output wire q
);
    wire t;
    assign t = d ^ q;
    t_ff uut (
        .t(t),
        .clk(clk),
        .rst(rst),
        .q(q)
    );
endmodule
```


- Test bench


```
module tb_d_ff_using_t;
    reg d;
    reg clk, rst;
    wire q;
    d_ff_using_t uut(
        .d(d),
        .clk(clk),
        .rst(rst),
        .q(q)
    );
    initial clk = 0;
    always #5 clk = ~clk;
    initial begin
        $dumpfile("d_ff_using_t.vcd");
        $dumpvars(0, tb_d_ff_using_t);
        d = 0; rst = 1;
        #10 rst = 0;
        d = 0; #10;
        d = 1; #10;
        d = 0; #10;
        d = 1; #10;
        d = 1; #10;
        d = 0; #10;

        $finish;
    end
    initial begin
        $monitor("Time=%0t | D=%b | Q=%b", $time, d, q);
    end
endmodule
```

II VVP output Screenshot


```
C:\iverilog\bin\Week5>vvp dsn
VCD info: dumpfile d_ff_using_t.vcd opened for output.
Time=0 | D=0 | Q=0
Time=20 | D=1 | Q=0
Time=25 | D=1 | Q=1
Time=30 | D=0 | Q=1
Time=35 | D=0 | Q=0
Time=40 | D=1 | Q=0
Time=45 | D=1 | Q=1
Time=60 | D=0 | Q=1
Time=65 | D=0 | Q=0
```

III GTKwave output screenshot

 

IV Truth Table

Current State	D Input	Required T Input	T Flip-Flop Action	Next State
Q_n	D	$T = D \oplus Q_n$		Q_{n+1}
0	0	$0 \oplus 0 = 0$	Hold	0
0	1	$1 \oplus 0 = 1$	Toggle	1
1	0	$0 \oplus 1 = 1$	Toggle	0
1	1	$1 \oplus 1 = 0$	Hold	1

 Export to Sheets